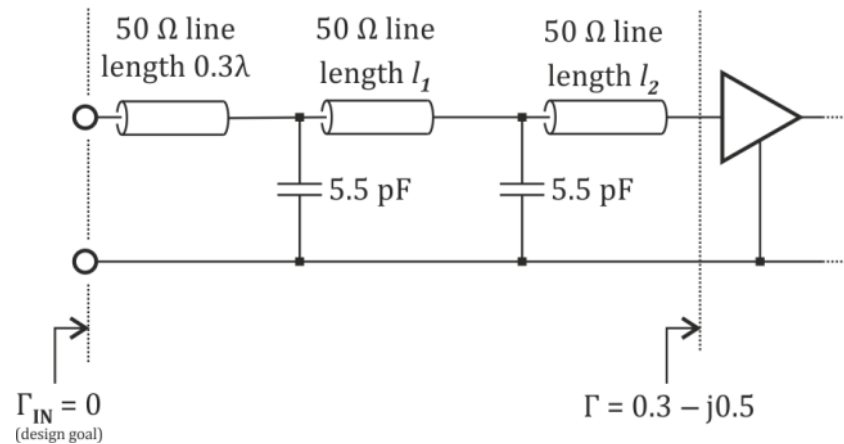



## 5. Matching of an RF Amplifier Module - Reference Solution

The input of an RF amplifier module operating at  $f_c = 1$  GHz shows a reflection coefficient  $\Gamma = 0.3 - j0.5$ . By means of two 5.5 pF capacitors, placed along a lossless 50  $\Omega$  line, the input of the entire circuit shall be matched to 50  $\Omega$ .



By using the Smith-chart determine the transmission line lengths  $l_1$  and  $l_2$  (as a ratio of the wavelength  $\lambda$ )!

## 5. Matching of an RF Amplifier Module - Reference Solution

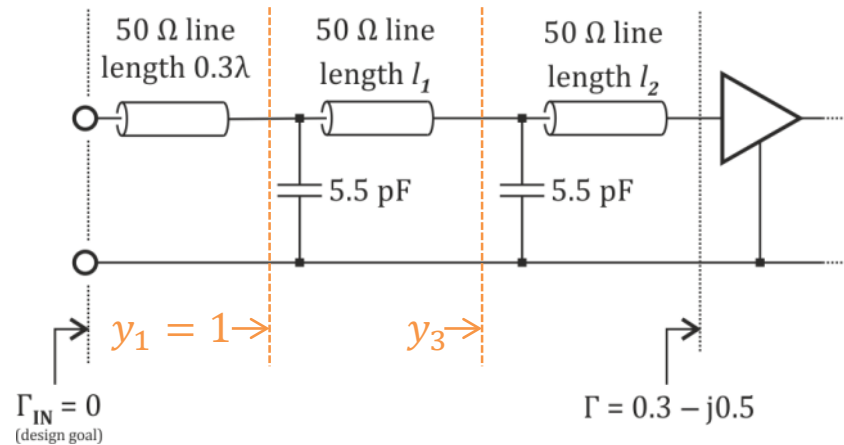**50 Ω line (with length  $0.3\lambda$ ) at the input can be ignored...**

...because it has the same impedance as the desired input impedance.

**Solution approach:**


1. divide the network into two parts by a reference plane located in between the adjustable elements
2. determine the set of admittances  $y_3$  which can be matched to  $y_1 = 1$  (equ. 50 Ω) by the left-hand side network (5.5pF + line 1)
3. determine the set of admittances  $y_3$  which can be realized by the right-hand side network (5.5pF + line 2 + amplifier)
4. intersect both sets to find a solution for  $y_3$
5. based on the solution for  $y_3$  determine the lengths of line 1 and line 2

**Info:** Because all lines (of which the reference planes are shifted along) have a wave impedance of 50 Ω, the Smith-chart used for the solutions is referenced to 50 Ω as well.


# 5. Matching of an RF Amplifier Module - Reference Solution
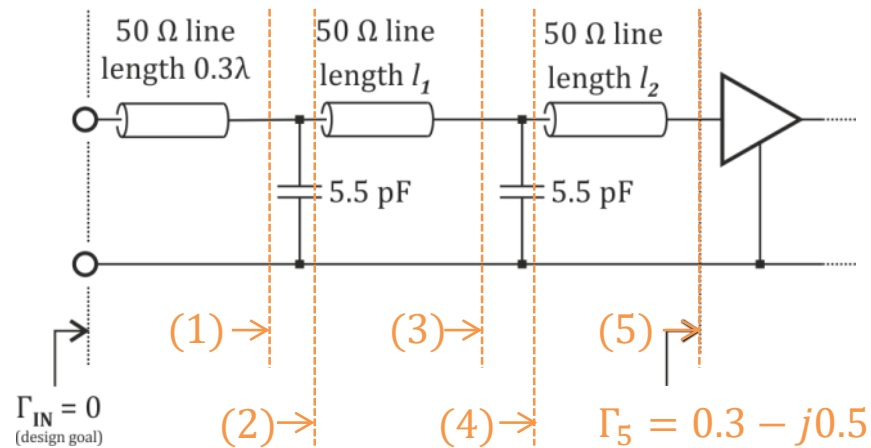
## The following notation will be used in the Smith-charts:

- impedances are marked in **BLUE**
- admittances are marked in **RED**
- construction steps are marked in **ORANGE**  
(sometimes other colors might also be used for clarity)
- the reference impedance is indicated in to upper left corner
- pastel colors are used for preceding construction steps, impedances, and admittances
- reference planes are denoted by (1),(2),(3),(4) and (5);  
they are located at the following positions and use the following orientations:




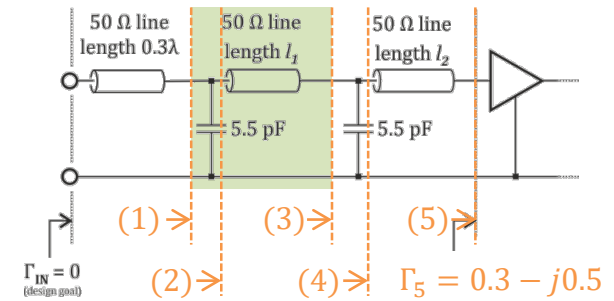
# 5. Matching of an RF Amplifier Module - Reference Solution



We start by determining the set of admittances  $y_3$  which can be matched to  $y_1 = 1$  (equ.  $50 \Omega$ ) by the network marked in green ( $5.5\text{pF} + \text{line } 1$ )...

# 5. Matching of an RF Amplifier Module - Reference Solution

$Z_0 = 50\Omega$

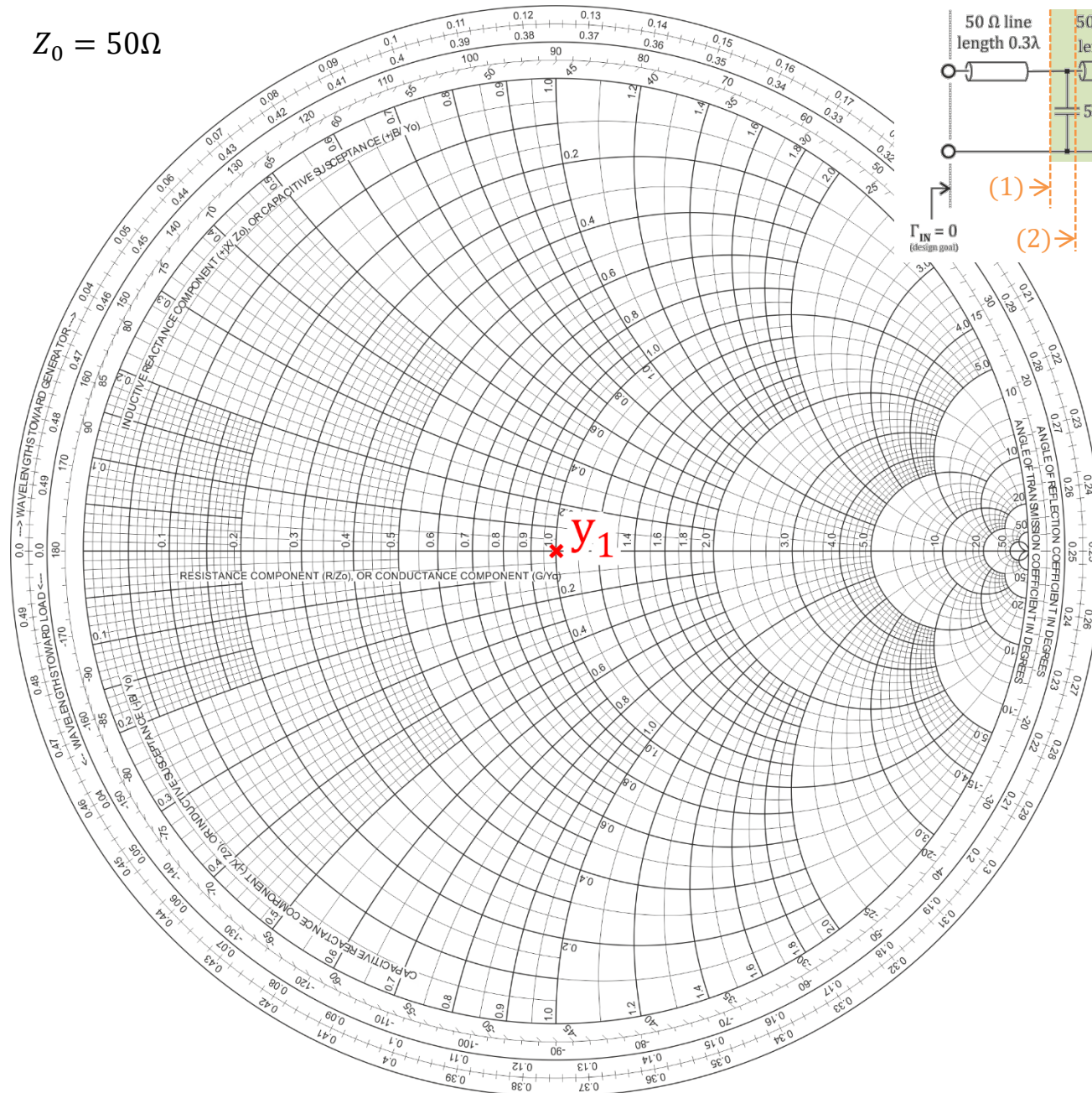
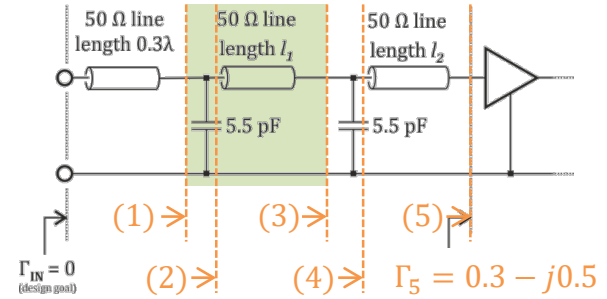


Solution for left part (5.5pF + line 1):

- **enter  $y_1$**  (use admittance plane because when shifting the reference plan to  $y_2$  we have to deal with a parallel connection of the 5.5pF capacitor)

# 5. Matching of an RF Amplifier Module - Reference Solution

$$Z_0 = 50 \Omega$$

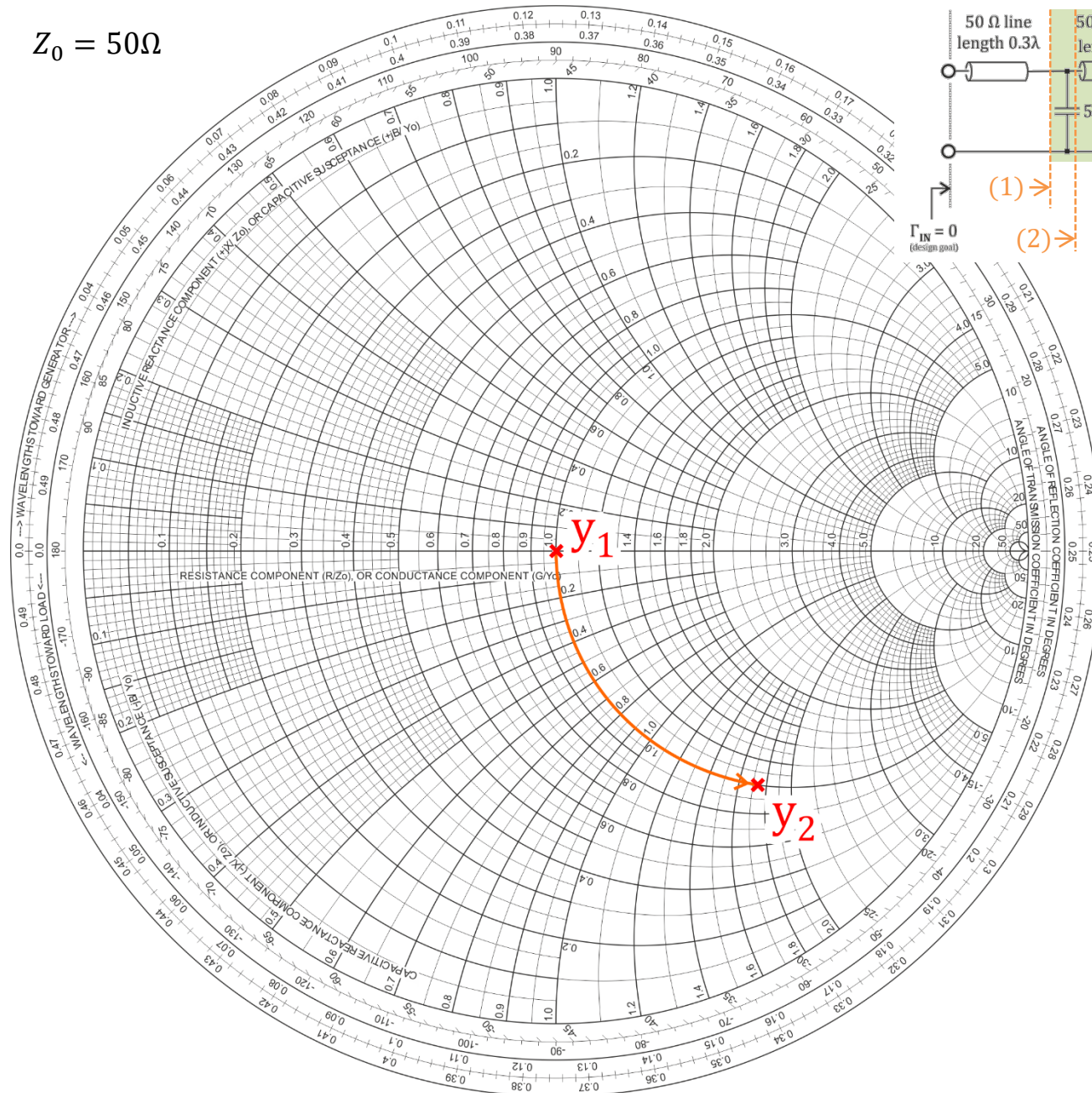
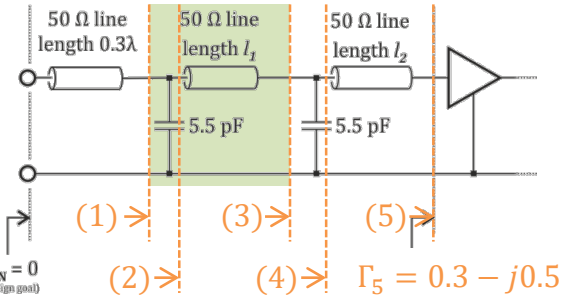


**Solution for left part (5.5pF + line 1):**

- enter  $y_1$
- **shift reference plane  $y_1$  to  $y_2$  by removing the 5.5pF capacitor (this equals a subtraction of the admittance!)**
- $$y_c = \frac{Z_0}{Z_c} = j\omega C Z_0 = +j1.73$$

# 5. Matching of an RF Amplifier Module - Reference Solution


$Z_0 = 50\Omega$

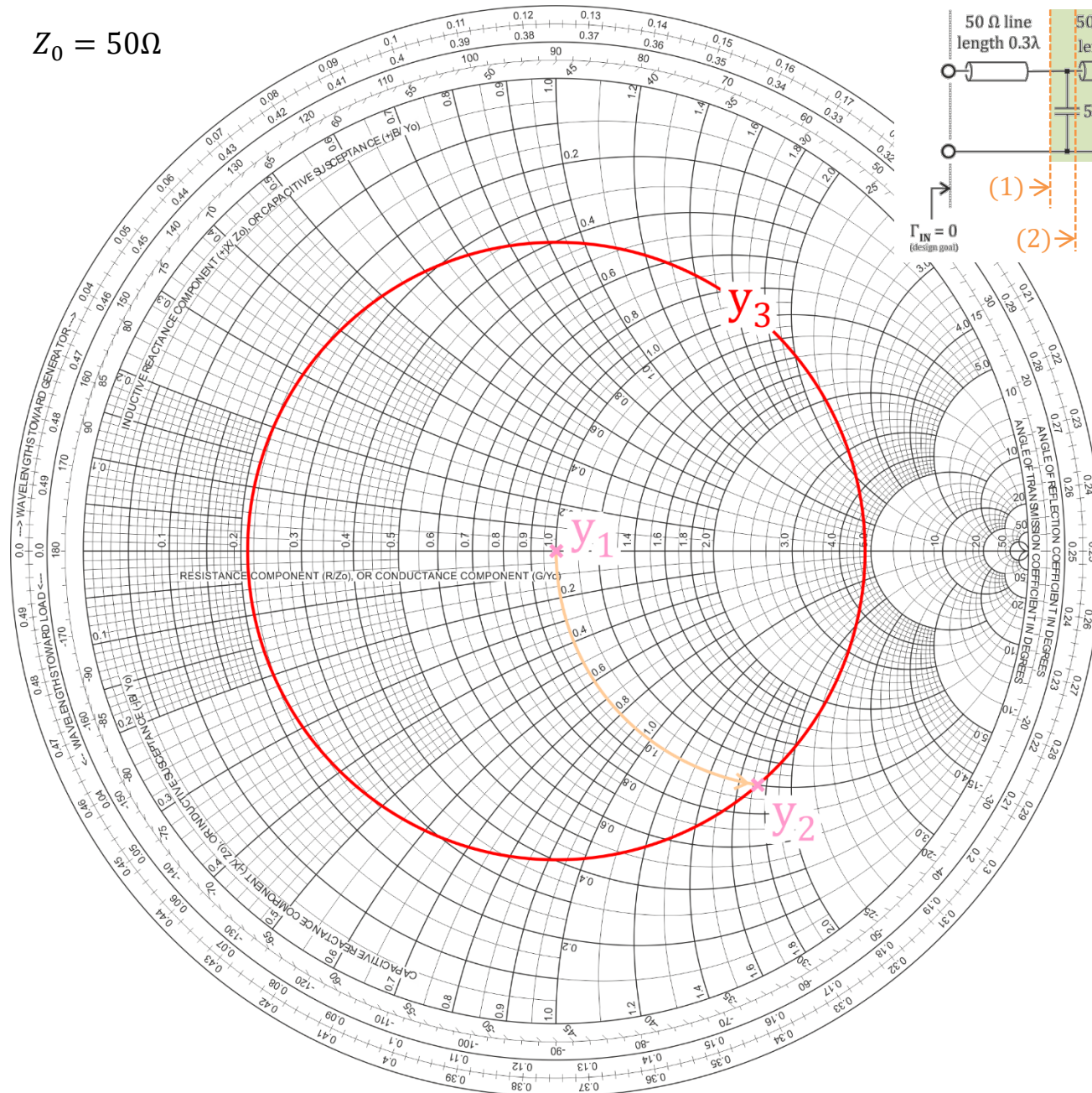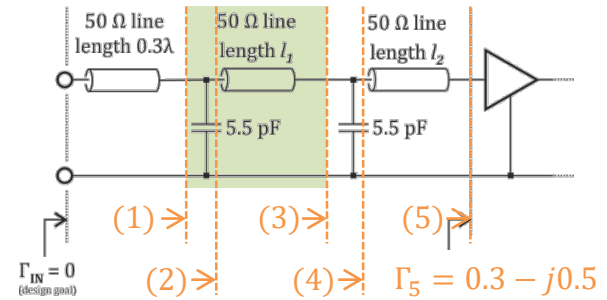

## Solution for left part (5.5pF + line 1):

- enter  $y_1$
- shift reference plane  $y_1$  to  $y_2$  by removing the 5.5pF capacitor
- **shift reference plane  $y_2$  to  $y_3$**  (this is done by rotating  $y_2$  towards the load along a circle)
- any admittance on the circle  $y_3$  can be matched to  $y_1 = 0$  by choosing an appropriate line length  $l_1$
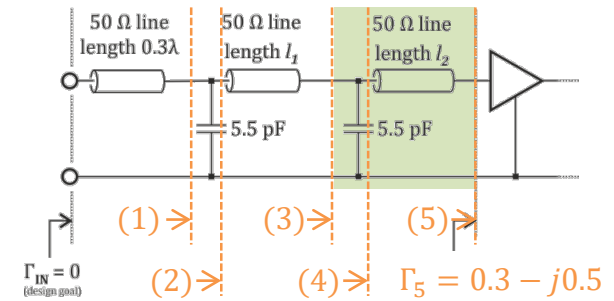
# 5. Matching of an RF Amplifier Module - Reference Solution





Next, we determine the set of reflection coefficients  $\gamma_3$  which can be realized by the network marked in green (5.5pF + line 2 + amplifier)...



# 5. Matching of an RF Amplifier Module - Reference Solution

$$Z_0 = 50\Omega$$

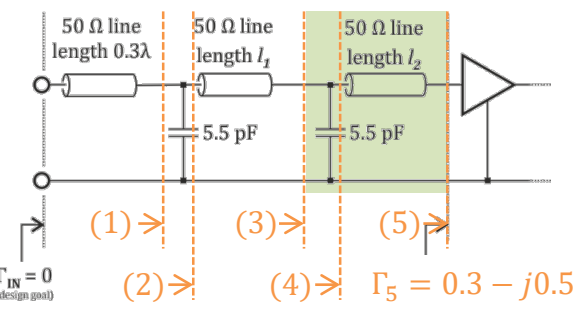
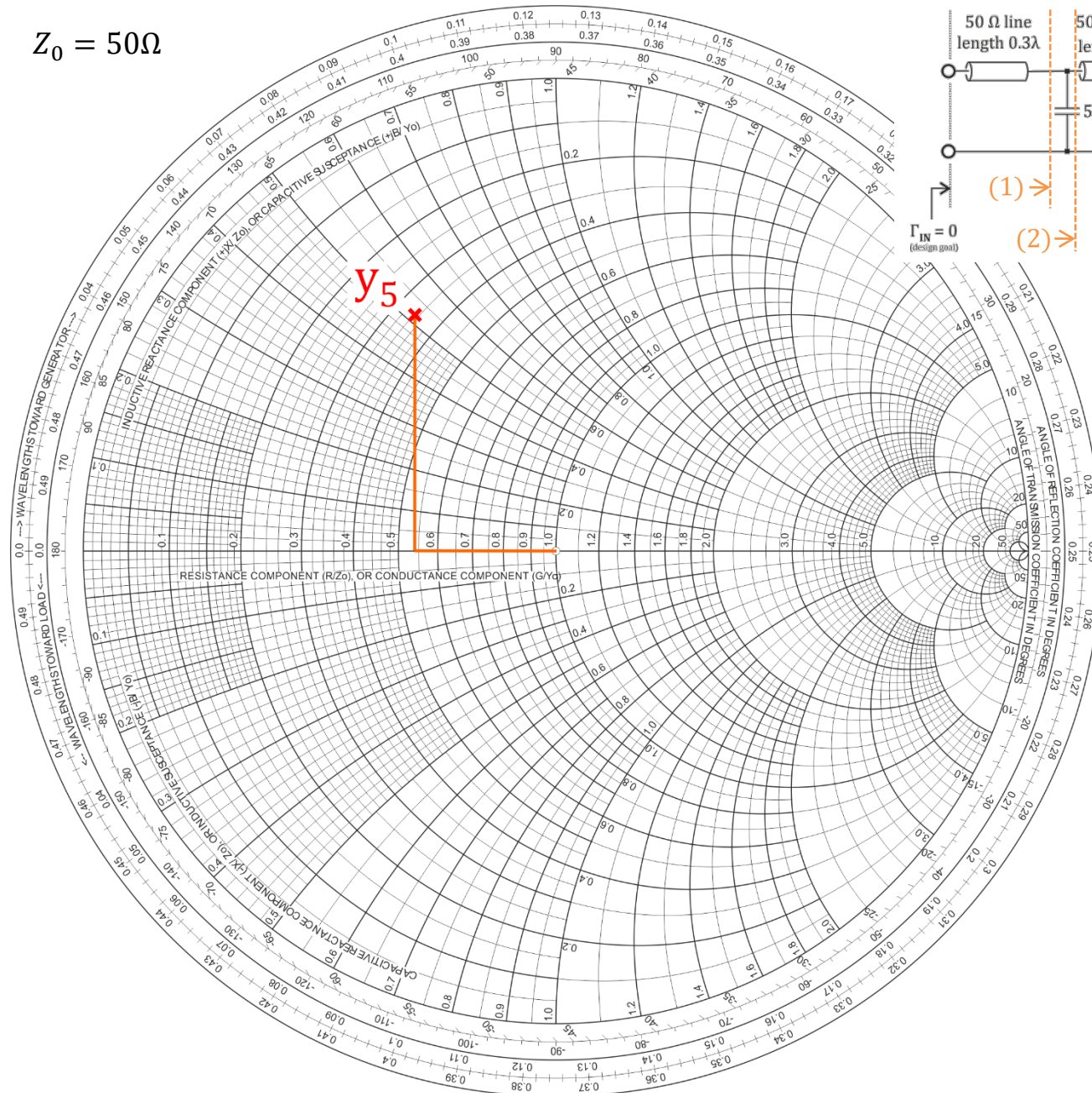


Solution for right part (5.5pF + line 2 + amp):

- **enter  $y_5$**   
( $\Gamma_5 = 0.3 - j0.5$ )  
again, use admittance plane because later on we have to deal with a parallel 5.5pF capacitor

# 5. Matching of an RF Amplifier Module - Reference Solution

$$Z_0 = 50 \Omega$$

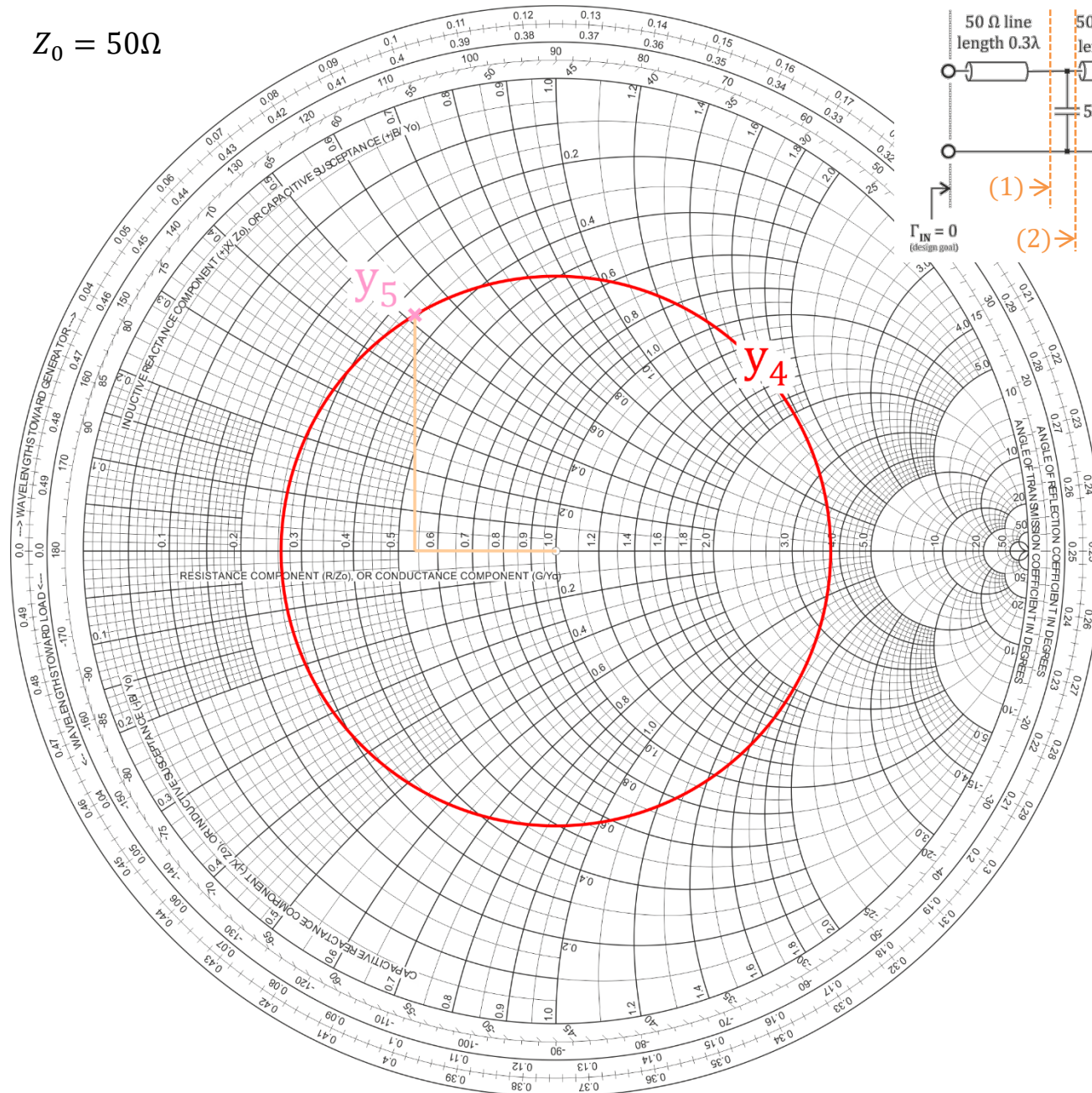
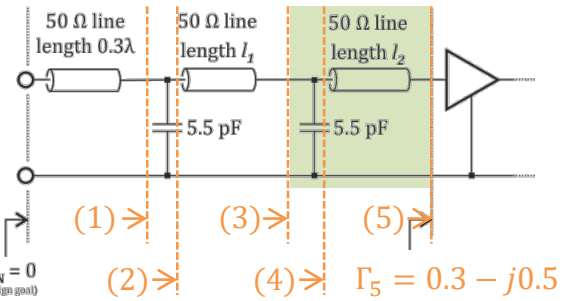


**Solution for right part (5.5pF + line 2 + amp):**

- enter  $y_5$
- **shift reference plane  $y_5$  to  $y_4$**  (this is done by rotating  $y_5$  towards the generator along a circle)
- any admittance on the circle  $y_4$  can be realized by choosing different line lengths  $l_2$

# 5. Matching of an RF Amplifier Module - Reference Solution

$$Z_0 = 50\Omega$$

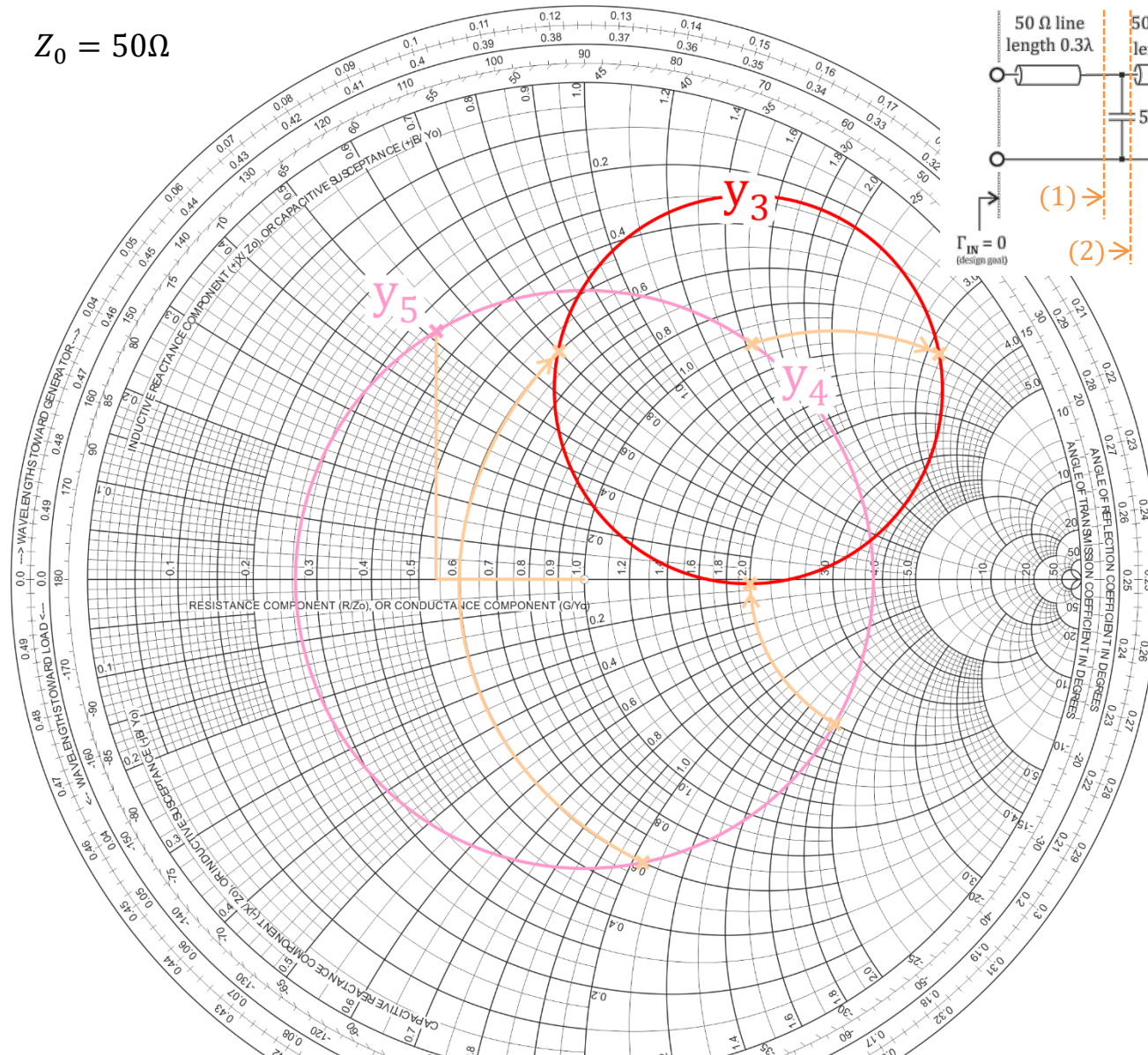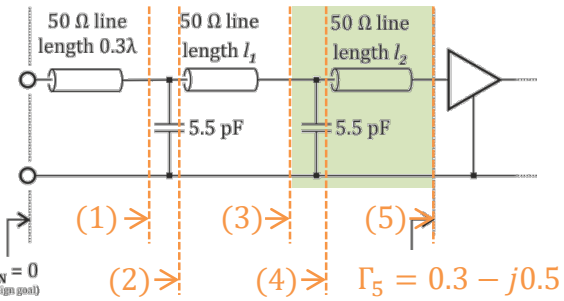


**Solution for right part (5.5pF + line 2 + amp):**

- enter  $y_5$
- shift reference plane  $y_5$  to  $y_4$
- **add the 5.5pF capacitor's admittance in order to determine the set of possible  $y_3$ 's**
- By knowing that this will result in a circle\*, three arbitrary points on the  $y_4$  circle are chosen, the capacitor's admittance is added, and the  $y_3$  circle is constructed then

\* The Smith-chart is a conformal mapping between  $\Gamma$ -plane (reflection coefficients) and the  $Y/Z$ -plane (= it preserves angles). Circles will be transformed into circles. When adding constant imaginary values to the reflection coefficient this corresponds to a parallel movement of the circle in  $Y$ -plane and, therefore, results in a circle in the  $\Gamma$ -plane again.


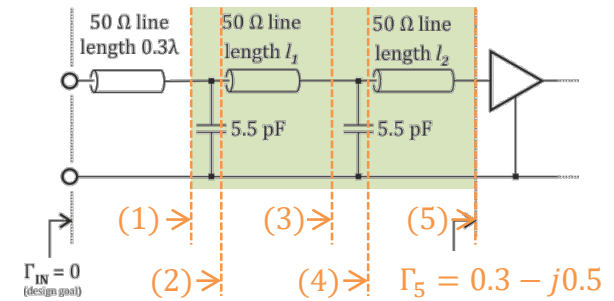
# 5. Matching of an RF Amplifier Module - Reference Solution



Now, as we have solutions for  $y_3$  based on the left and right half of the circuit, we determine a  $y_3$  which can be matched by the left circuit to 50  $\Omega$  and can be realized by the right one...


# 5. Matching of an RF Amplifier Module - Reference Solution

$Z_0 = 50 \Omega$

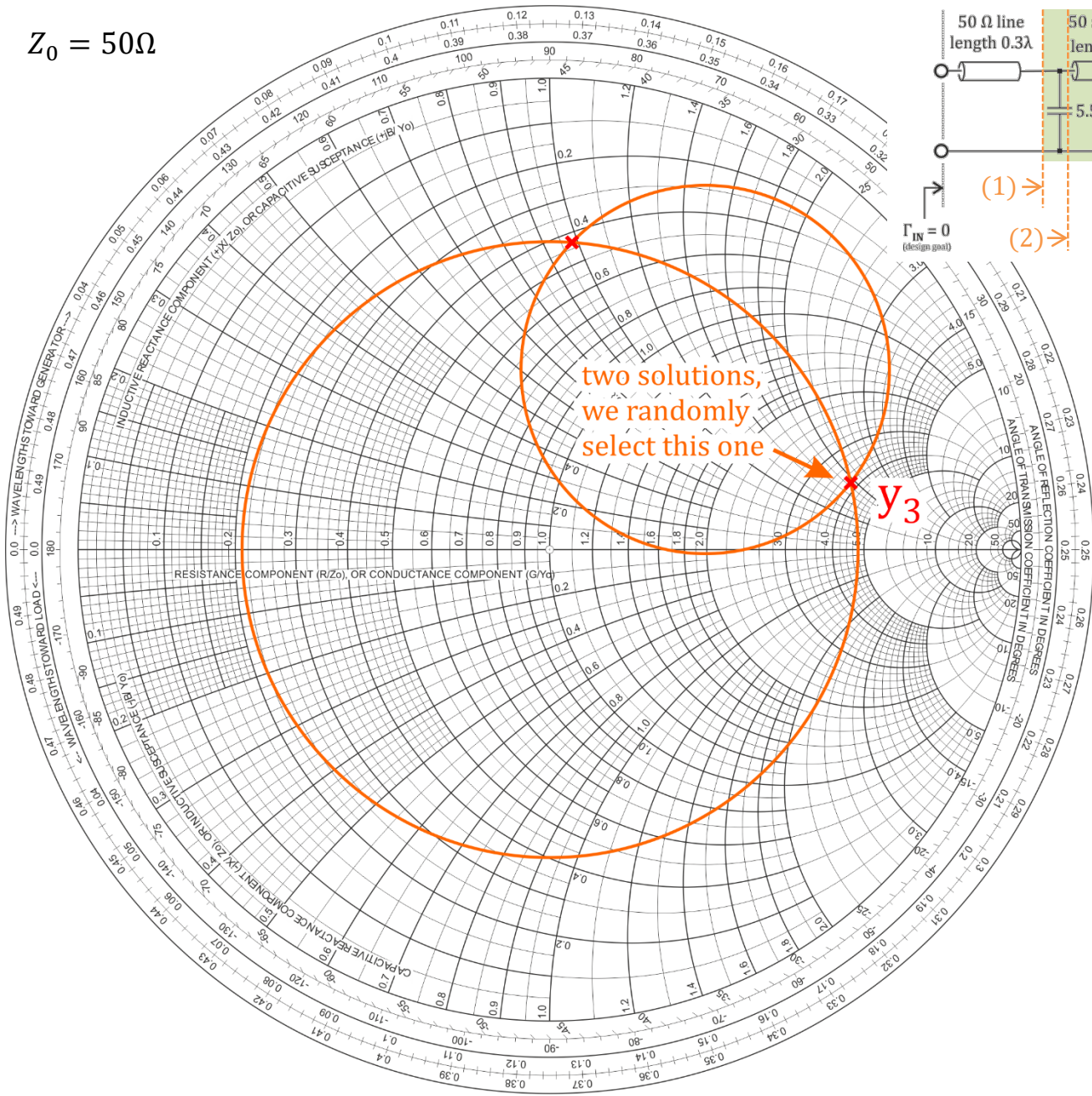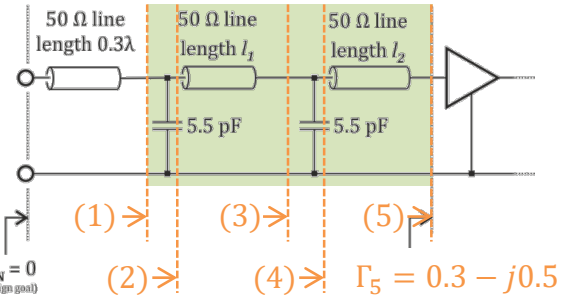

- intersect the solution-sets of  $y_3$  (the one for the left and the one for the right half) to find a solution for  $y_3$
- two solutions!
- both solutions are valid, we decide to go for the depicted one


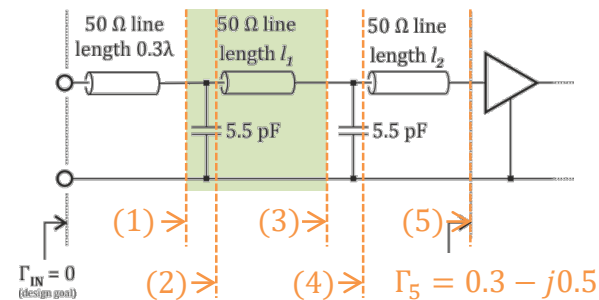
# 5. Matching of an RF Amplifier Module - Reference Solution



Next, as we know the value  $y_3$  we get back to the solution of the left-hand circuit and determine the length of line 1...

# 5. Matching of an RF Amplifier Module - Reference Solution

$Z_0 = 50 \Omega$

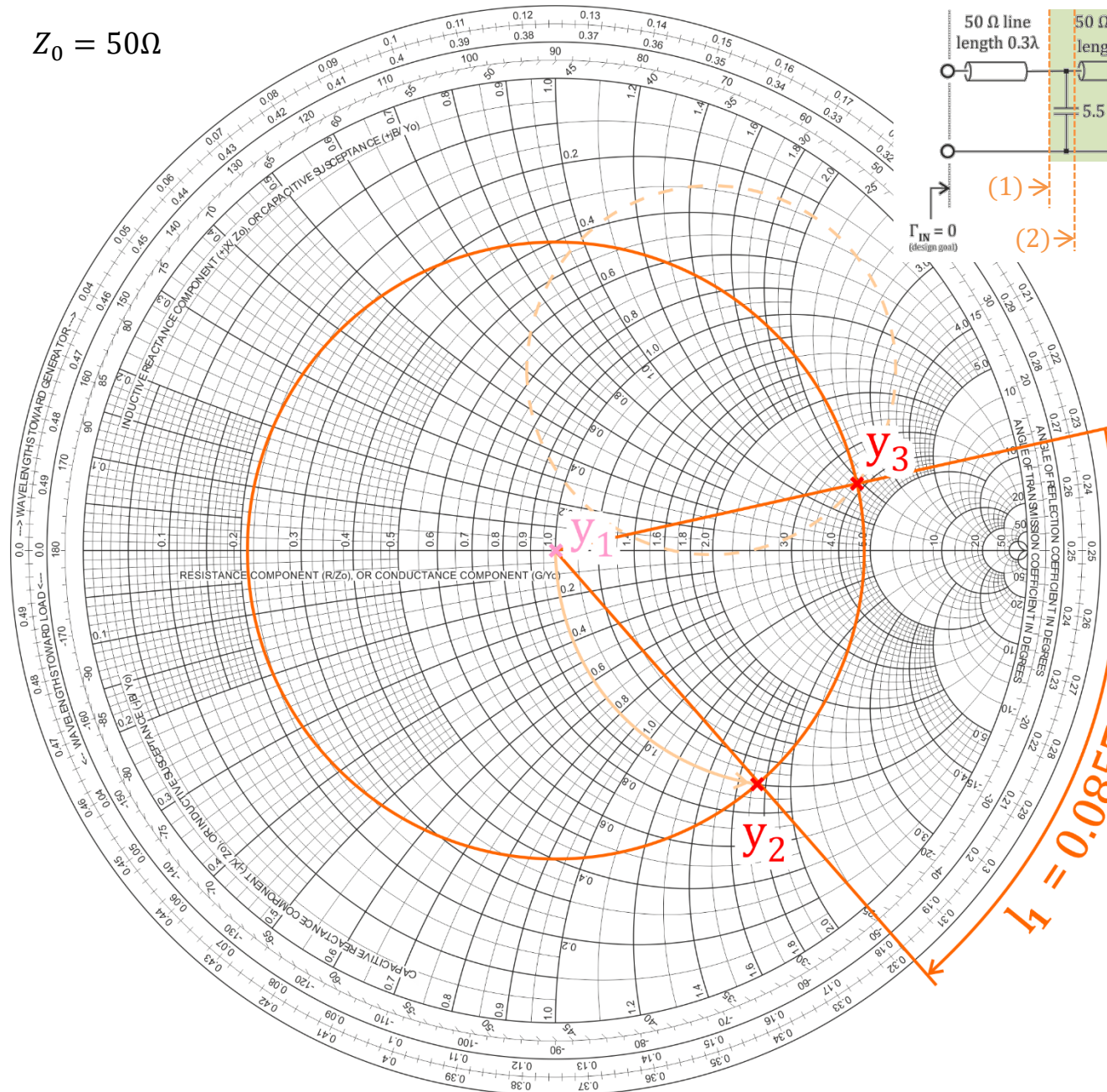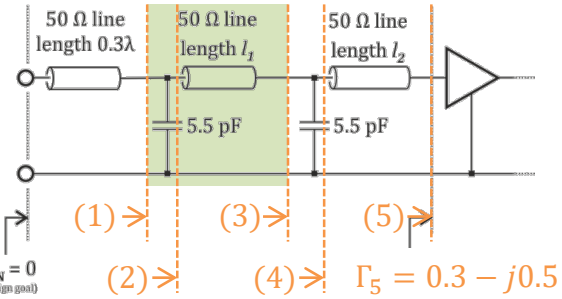


Solution for the left part (5.5pF + line 1):

- enter  $y_3$  in the solution for the left circuit half (5.5pF + line 1)
- determine the length of line 1 by the required rotation of  $y_3$  along the line 1 towards the generator in order to achieve  $y_2$

$l_1 = 0.0857 \lambda$

$\rightarrow l_1 = 0.0857 \lambda$
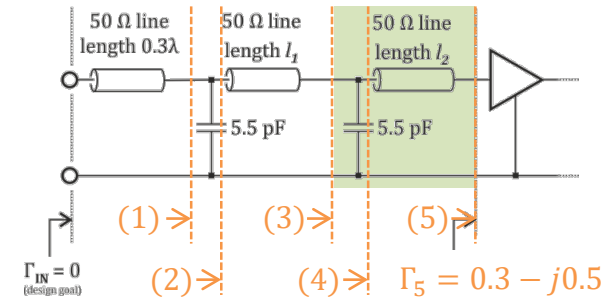
# 5. Matching of an RF Amplifier Module - Reference Solution





Now, we determine the length of line 2 by entering the found  $y_3$  value in the solution of the circuit's right half...



# 5. Matching of an RF Amplifier Module - Reference Solution

$$Z_0 = 50\Omega$$

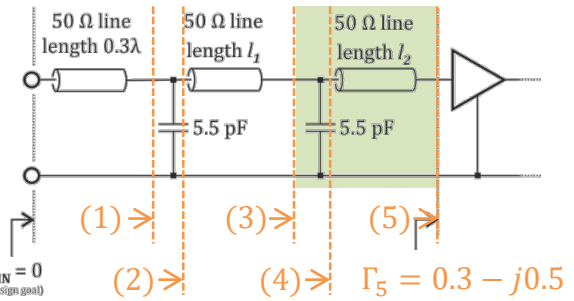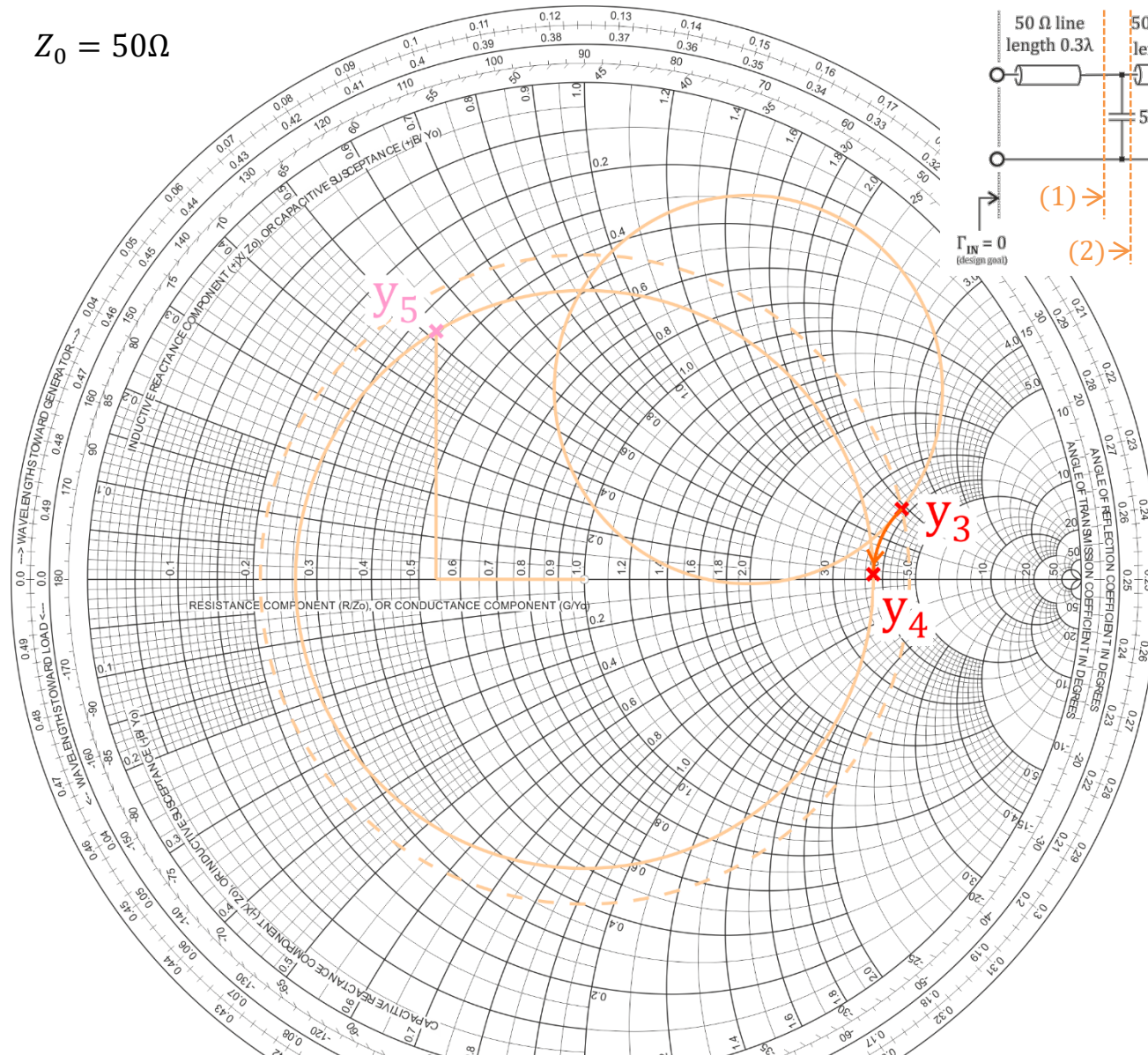

Solution for the right part (5.5pF + line 2 + amp):



- enter  $y_3$  in the solution for the right circuit half
- determine  $y_4$  by subtracting\*  $y_c$  from  $y_3$
- In case you forgot:  

$$y_c = \frac{Z_0}{Z_c} = j\omega CZ_0 = +j1.73$$

\* You need to subtract  $y_c$  from  $y_3$  out of the following reason: When measuring  $y_3$  the capacitor is included in the circuit. But when measuring  $y_4$  the capacitor needs to be removed. / Or think the other way round: If you know  $y_4$  you would have to add  $y_c$  in order to determine  $y_3$ . As we know  $y_3$  already,  $y_c$  needs to be subtracted.

# 5. Matching of an RF Amplifier Module - Reference Solution

$Z_0 = 50\Omega$

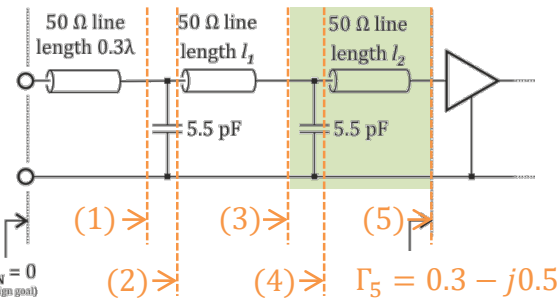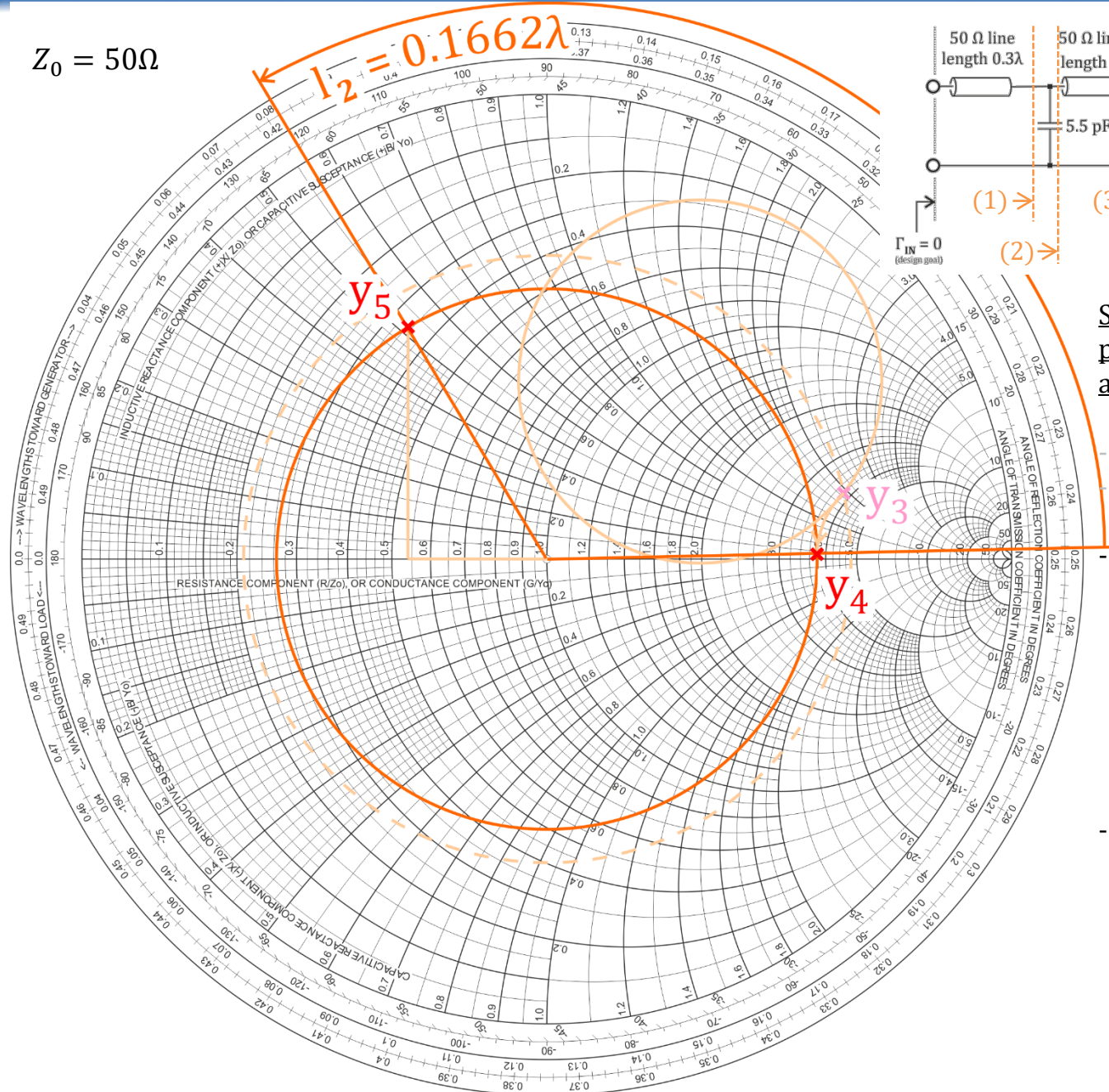

**Solution for the right part (5.5pF + line 2 + amp):**

- enter  $y_3$
- determine  $y_4$  by adding  $y_C$  to  $y_3$
- **determine the length of line 2** by the required rotation of  $y_3$  along the line 2 towards the load in order to achieve  $y_4$

**→  $l_2 = 0.1662\lambda$**

**That's it, you survived the tutorial!**

Questions?

Assoc. Prof. Dr. Holger Arthaber

Email: [holger.arthaber@tuwien.ac.at](mailto:holger.arthaber@tuwien.ac.at)

Room: CF0131