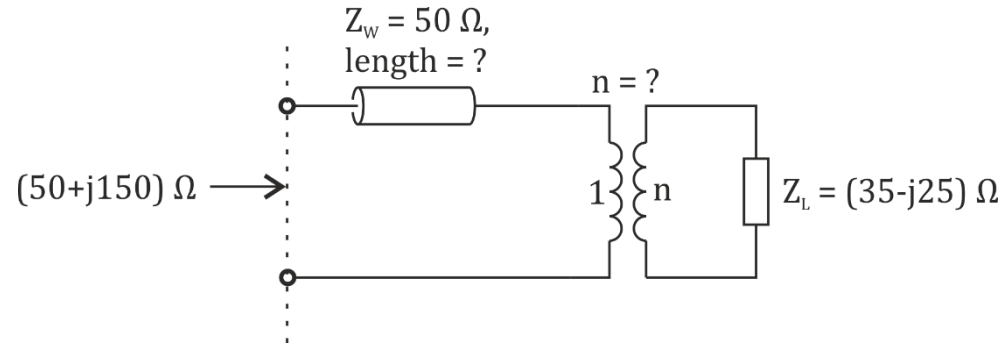


# 31. Impedance transformation - Reference Solution

The following circuit is to transform the load impedance  $Z_L$  into the given input impedance.




Use the Smith-Chart to determine the transformer's winding ratio and the line length (in fractions of the wavelength)!

Find the solution with the shortest possible transmission line length!

# 31. Impedance transformation - Reference Solution

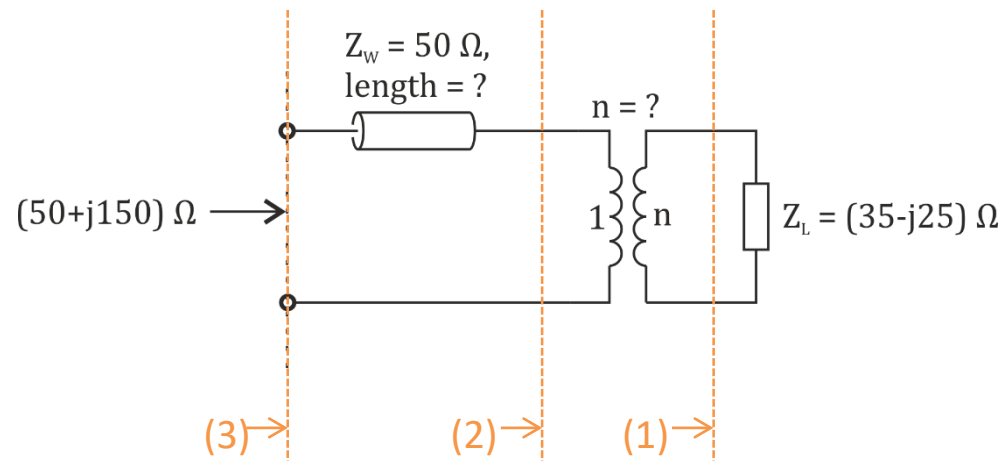
## The following notation will be used in the Smith-charts:

- impedances are marked in **BLUE**
- admittances are marked in **RED**
- construction steps are marked in **ORANGE**  
(sometimes other colors might also be used for clarity)
- the reference impedance is indicated in to upper left corner
- pastel colors are used for preceding construction steps, impedances, and admittances
- reference planes are denoted by (1),(2),(3);  
they are located at the following positions and use the following orientations:



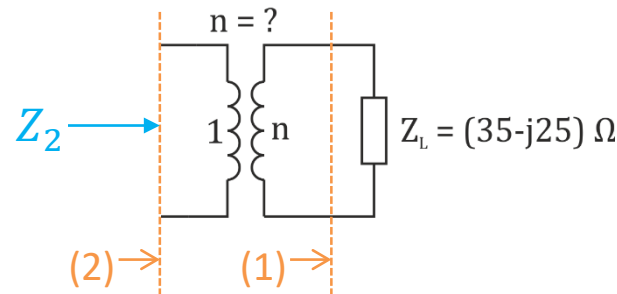
# 31. Impedance transformation - Reference Solution

How to handle a variable transformer in the Smith-chart?



→ The impedance  $Z_L$  is transformed to  $Z_2 = \frac{1}{n^2} Z_L$ .

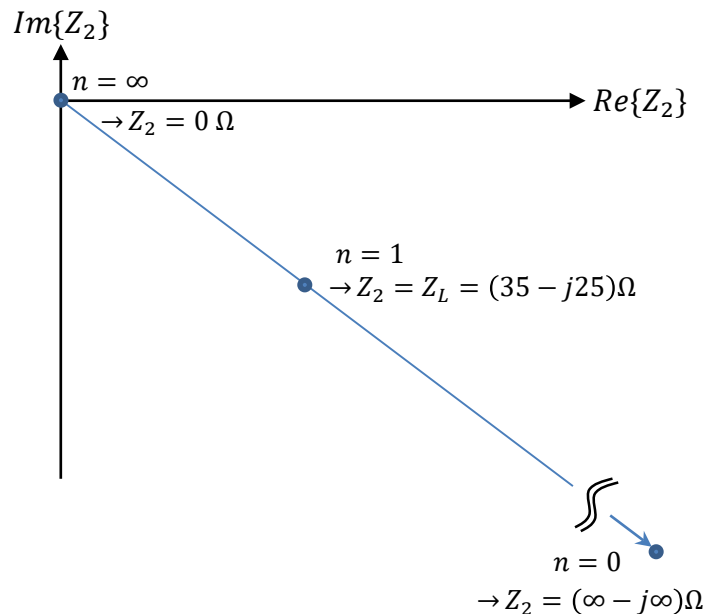→ The possible values of  $Z_2$  form a straight line in the Z-plane:





We know from other examples: ***Circles or lines (which are infinite radius circles) always transform into circles!***

Thus, we expect an arc in the Smith-chart going through

- $z = 0$  ( $\Gamma = -1$ ), short-circuit
- $z = \infty - j\infty$  ( $\Gamma = +1$ ), open
- $z = z_L$ , normalized  $Z_L$  impedance

# 31. Impedance transformation - Reference Solution

$$Z_0 = 50 \Omega$$

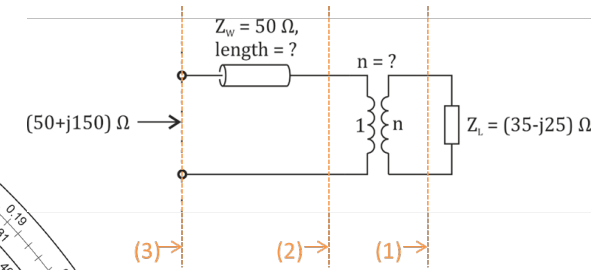
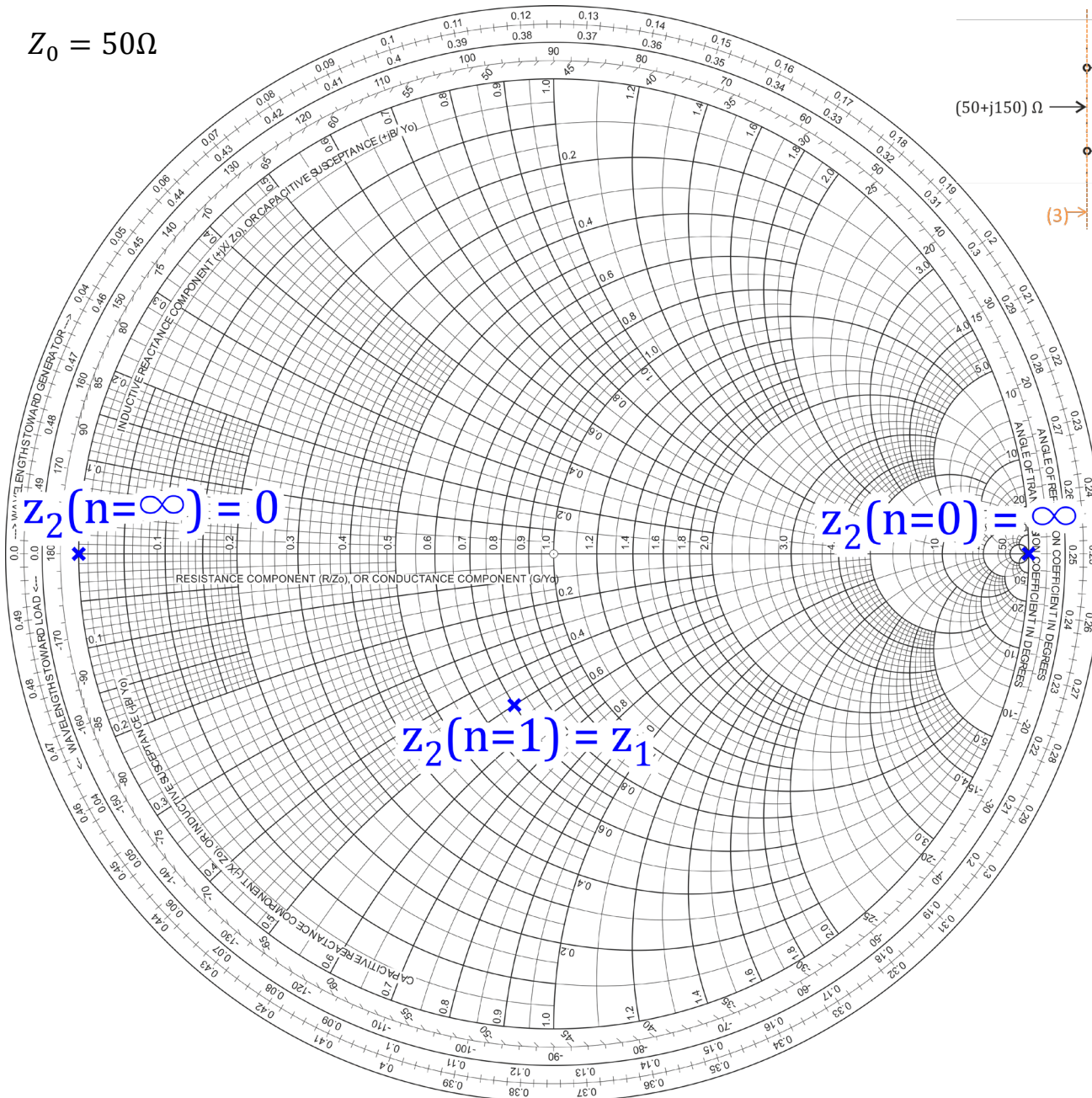


**Solution:**

- Enter three different values of  $z_2 = \frac{z_1}{n^2}$  (any values of  $n$  can be used)
- Use a  $50 \Omega$  Smith-chart (because of the line)

# 31. Impedance transformation - Reference Solution

$$Z_0 = 50 \Omega$$

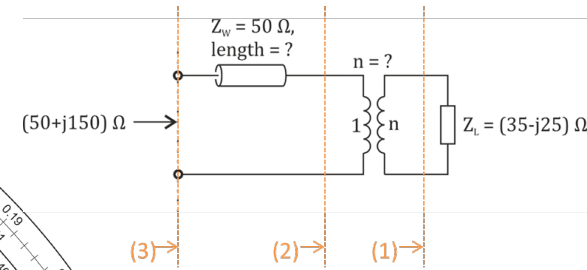
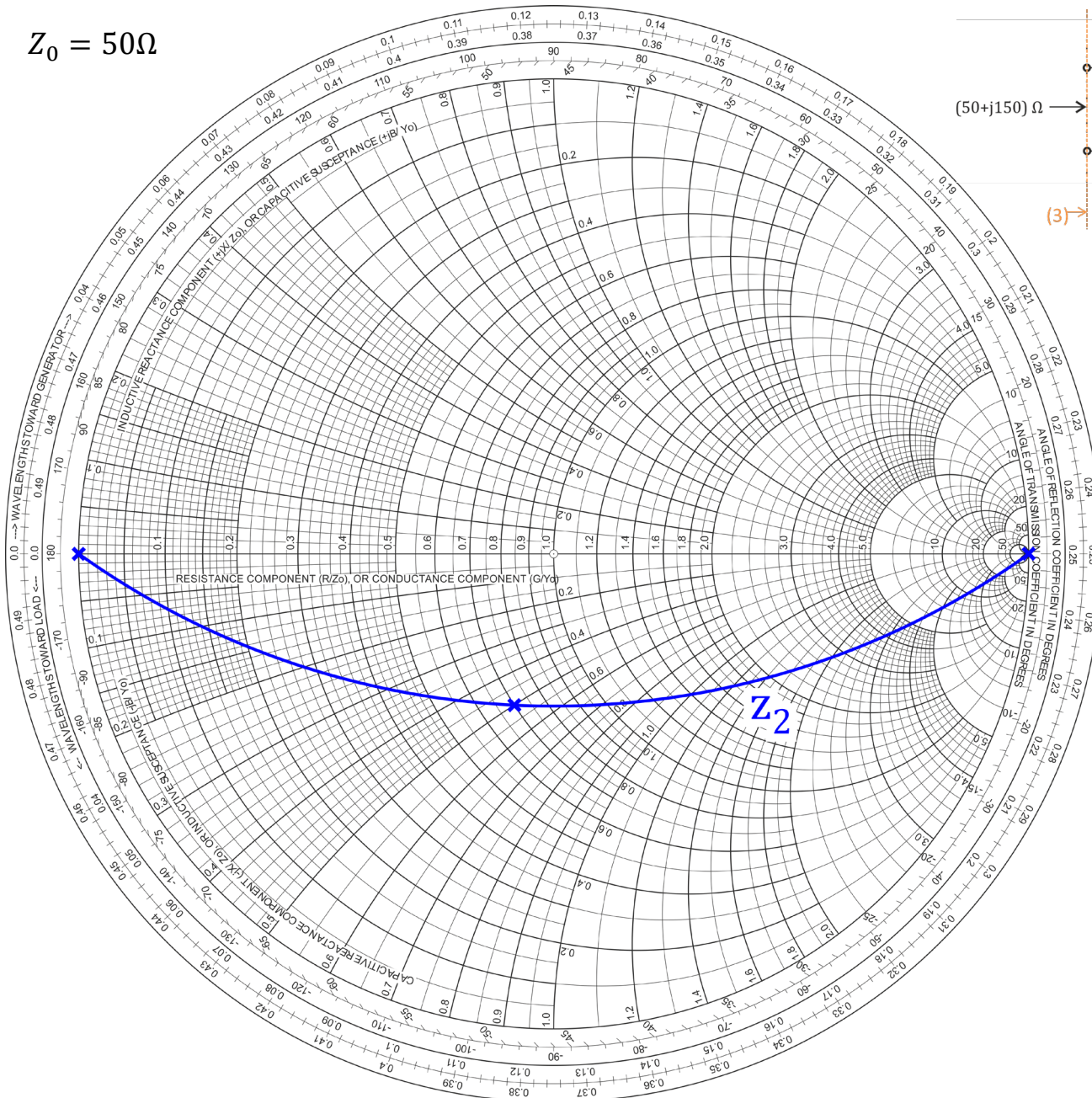


## Solution:

- Enter three different values of  $Z_2 = \frac{Z_1}{n^2}$
- **Construct an arc connecting those three points**  
*This arc shows all possible values of  $Z_2$  which can be achieved.*

# 31. Impedance transformation - Reference Solution

$$Z_0 = 50 \Omega$$

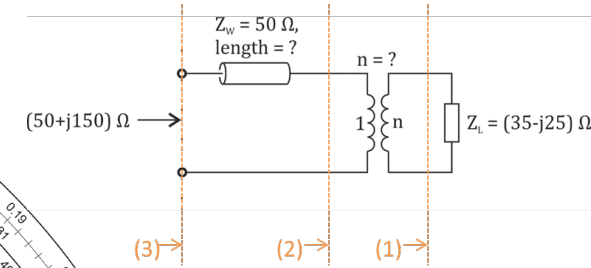
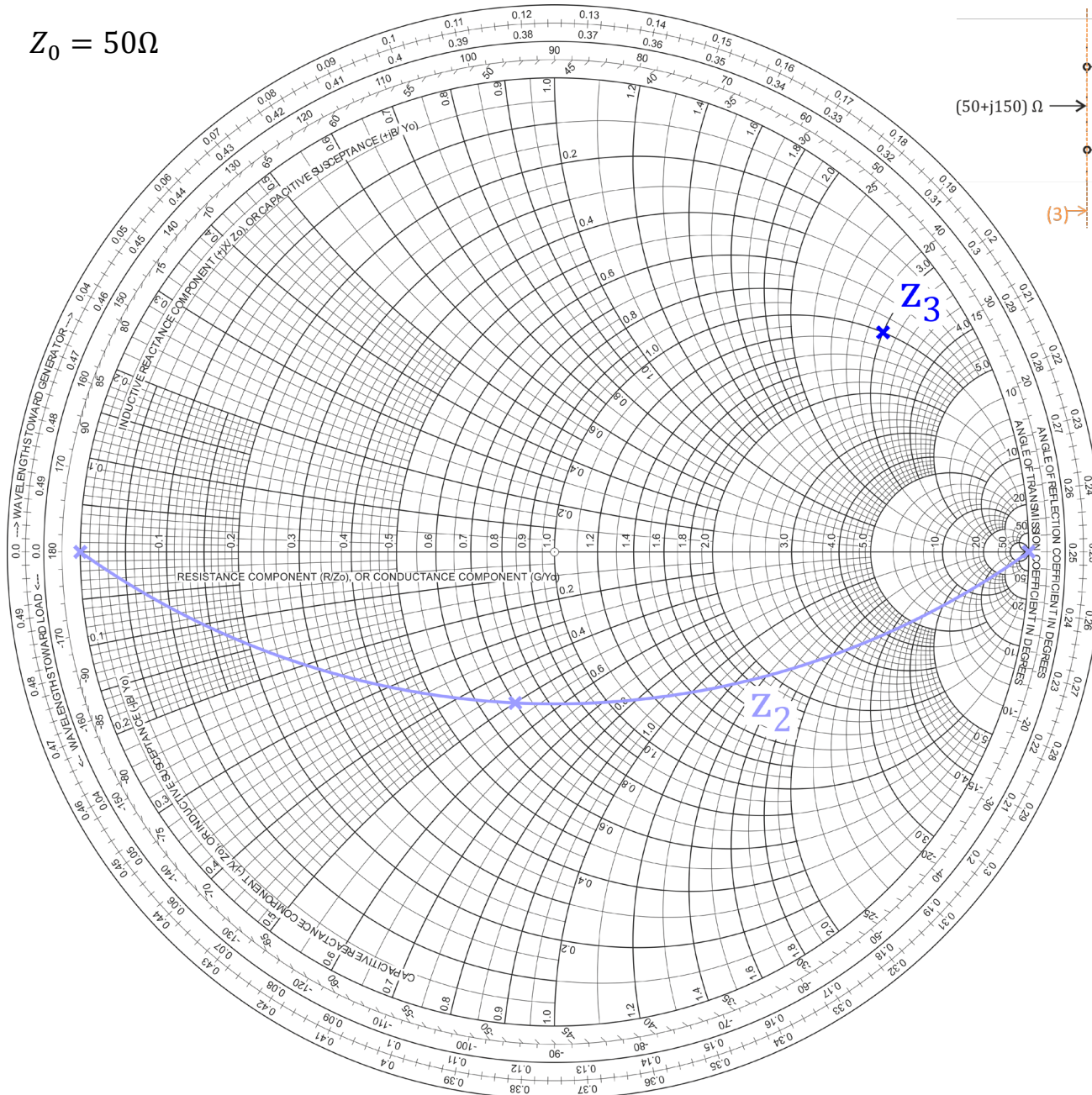


**Solution:**

- Enter three different values of  $Z_2 = \frac{Z_1}{n^2}$
- Construct an arc connecting those three points
- **Enter the targeted impedance  $Z_3 = 1 + j3$**

# 31. Impedance transformation - Reference Solution

$$Z_0 = 50 \Omega$$

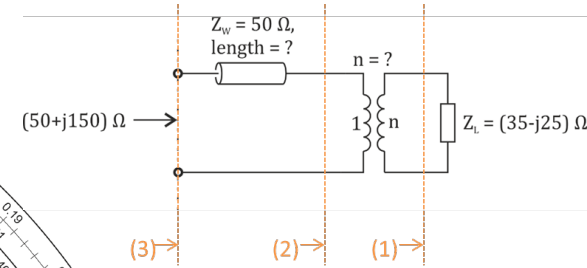
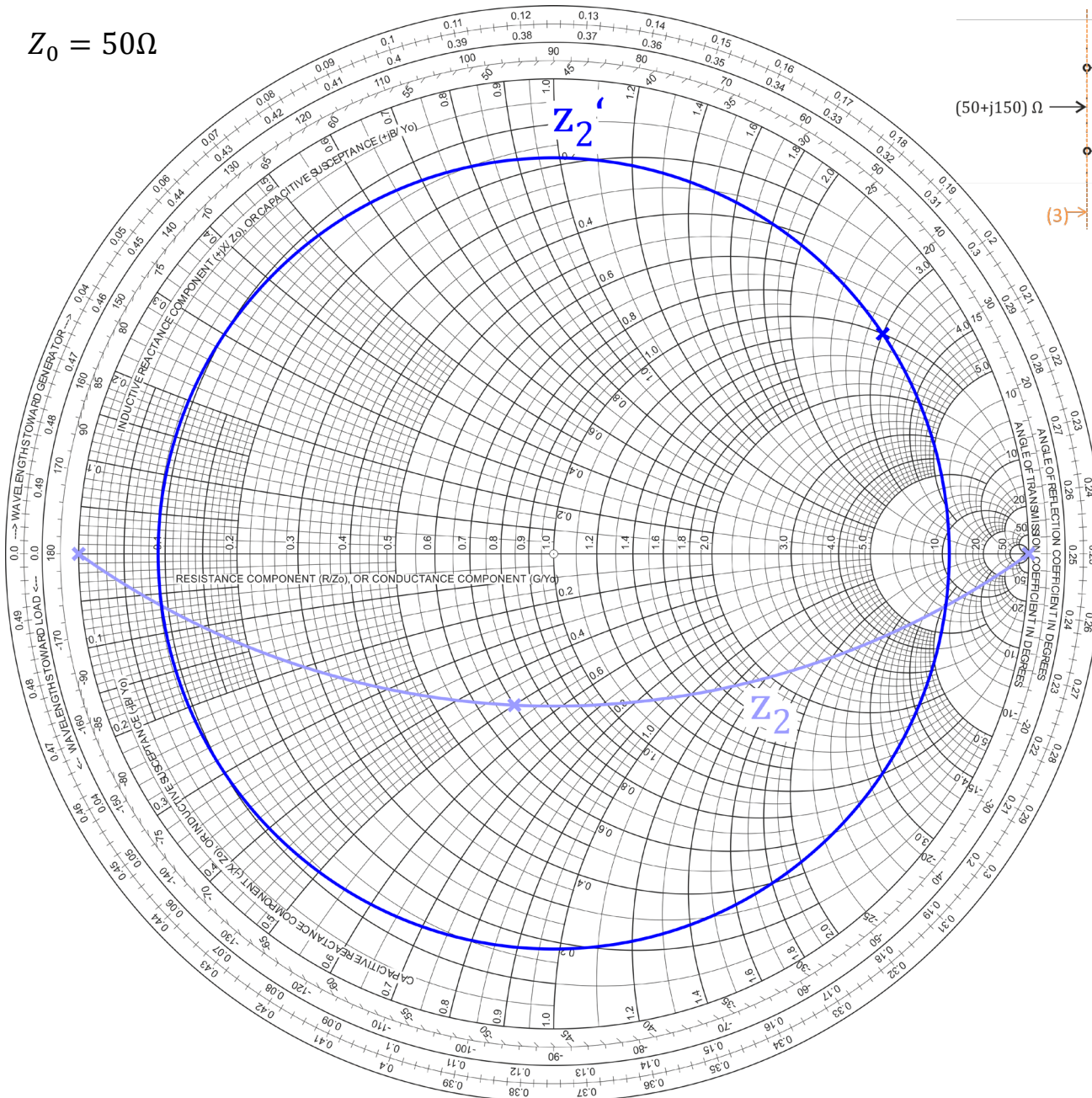


## Solution:

- Enter three different values of  $Z_2 = \frac{Z_1}{n^2}$
- Construct an arc connecting those three points
- Enter the targeted impedance  $Z_3 = 1 + j3$
- **Construct a circle of all impedances  $Z_2'$  which can be transformed into  $Z_3$  by a line**

# 31. Impedance transformation - Reference Solution

$$Z_0 = 50 \Omega$$

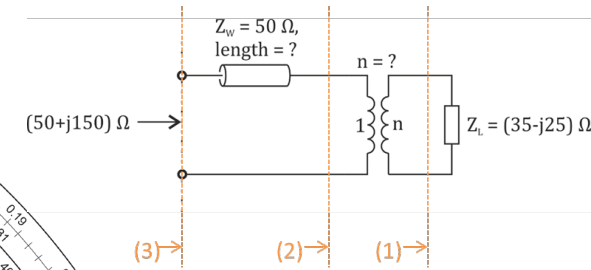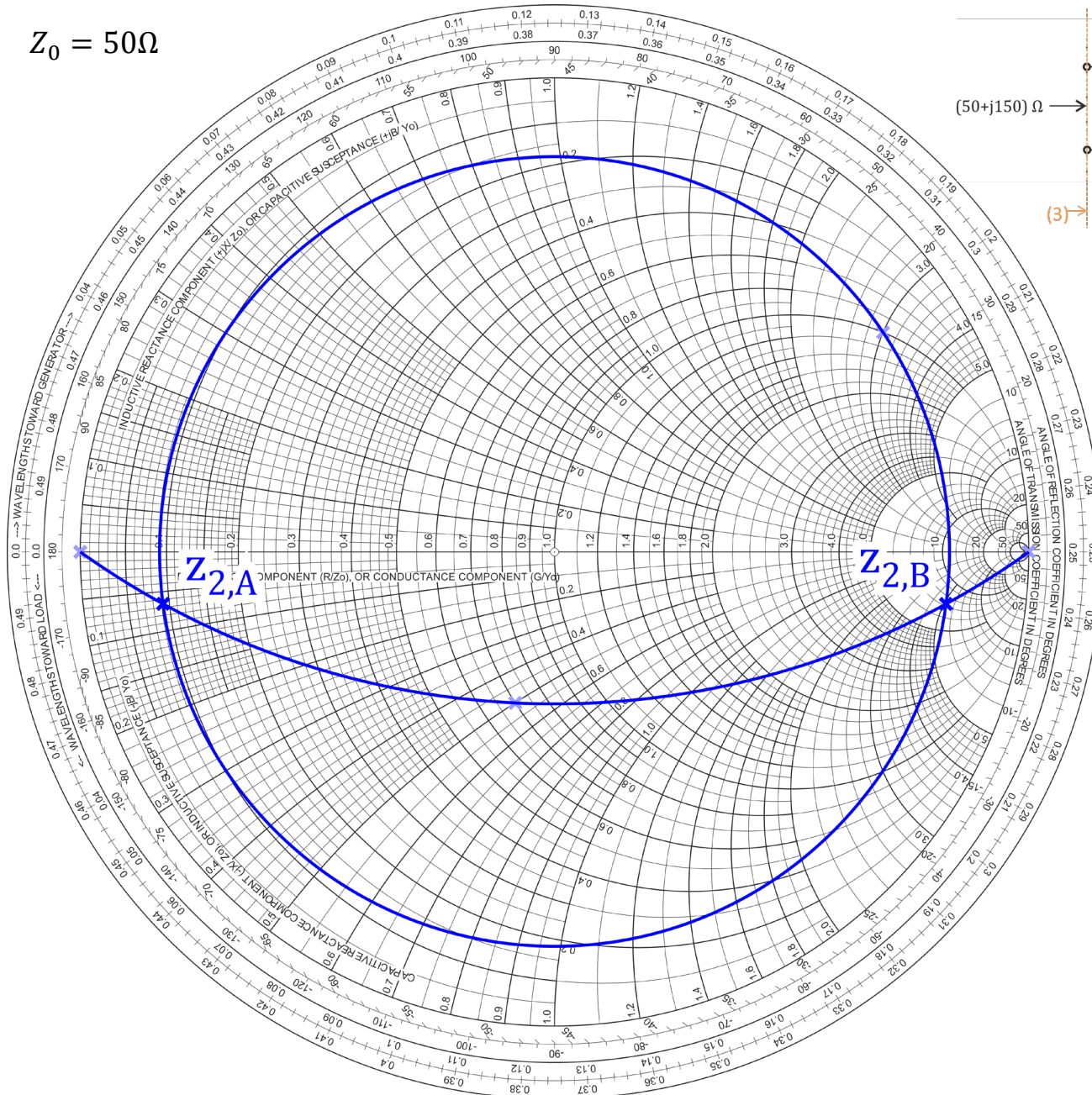



## Solution:

- Enter three different values of  $Z_2 = \frac{Z_1}{n^2}$
- Construct an arc connecting those three points
- Enter the targeted impedance  $Z_3 = 1 + j3$
- Construct a circle of all impedances  $Z_2'$  which can be transformed into  $Z_3$  by a line
- **Intersect the arc with the circle to find the two solutions  $Z_{2,A}$  and  $Z_{2,B}$**



# 31. Impedance transformation - Reference Solution

$$Z_0 = 50 \Omega$$

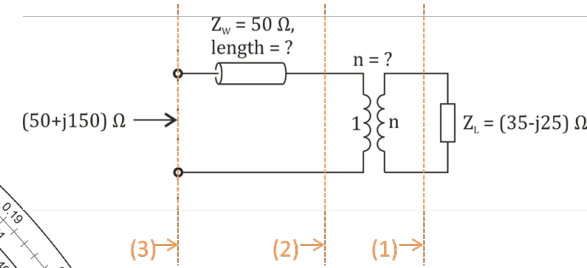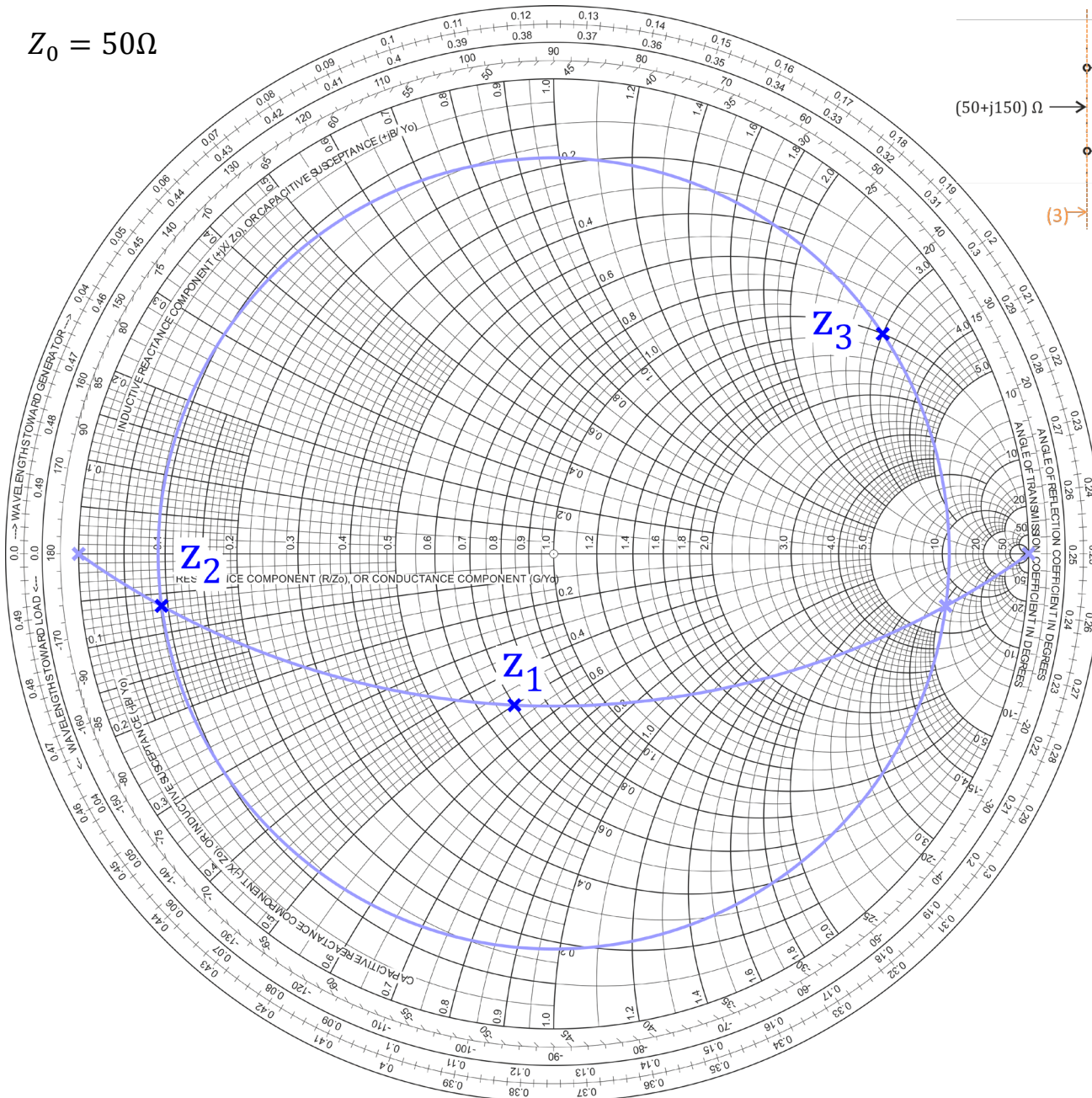

Get the transformation ratio  $n$ :

- Select solution  $z_{2,A}$  as it results in the shorter line length (see next slide for line length)
- Read impedance  $z_2 = 0.092 - j0.066$  and calculate



$$n = \sqrt{\frac{z_1}{z_2}} = \underline{2.757}$$

Info: There is no need to do a complex valued division – it is enough to compare either real- or imaginary-parts!

# 31. Impedance transformation - Reference Solution

$Z_0 = 50 \Omega$

$l = 0.214\lambda$

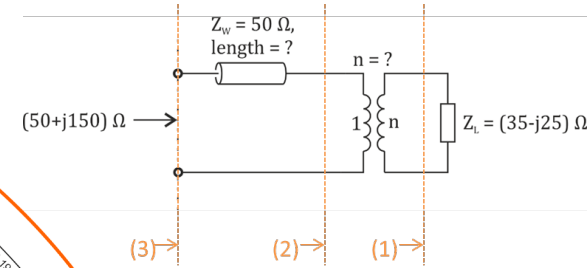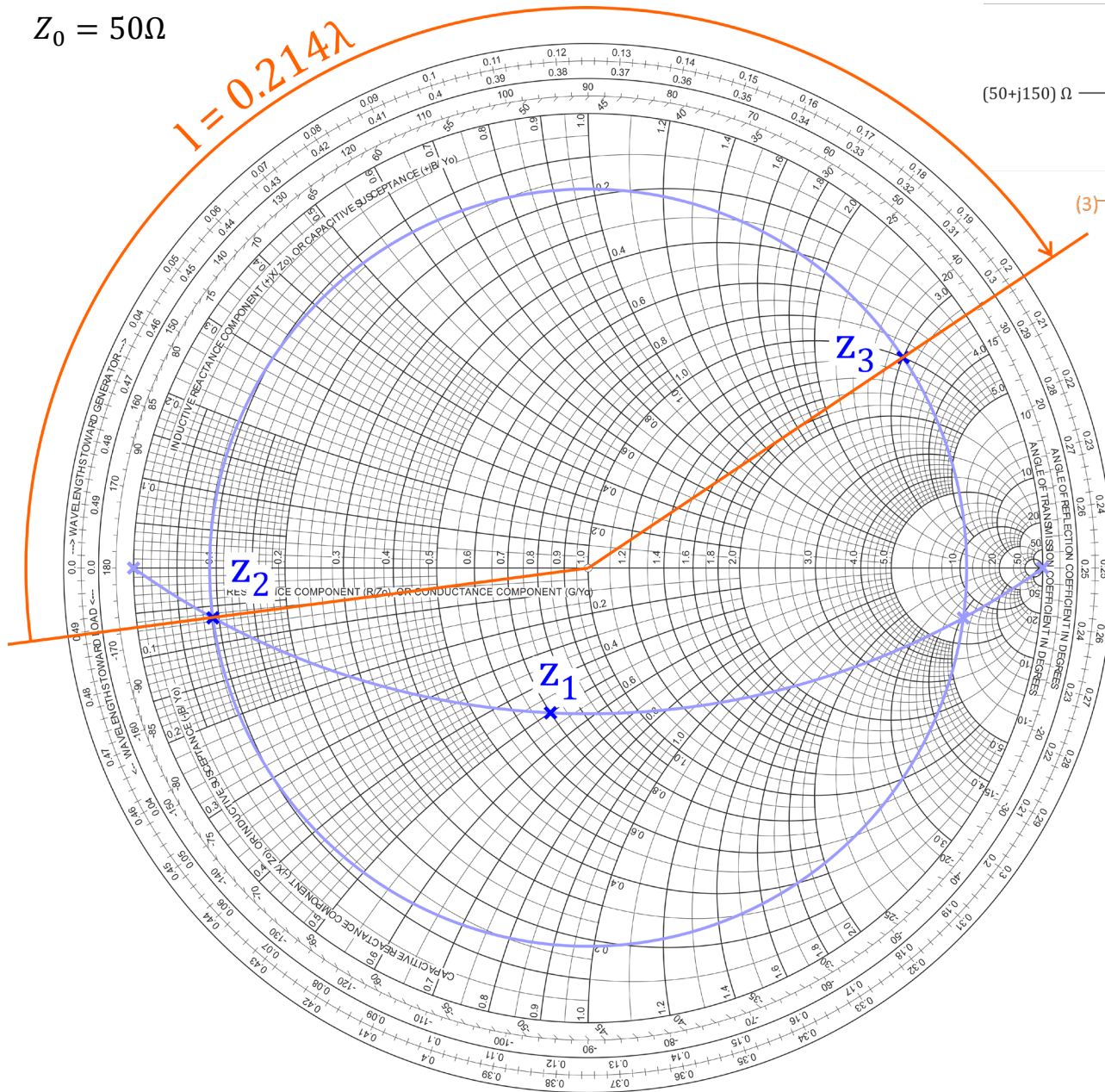

Get the line length:

- Determine the line length needed to transform  $z_2$  to  $z_3$  along the line towards the generator:  $l = \underline{0.214\lambda}$

**That's it, you survived the tutorial!**

Questions?

Assoc. Prof. Dr. Holger Arthaber

Email: [holger.arthaber@tuwien.ac.at](mailto:holger.arthaber@tuwien.ac.at)

Room: CF0131